

[illegible][illegible]

Power supply circuit diagram showing transformer terminals (X155, X156, X157, X158), switch SQ1, diode bridge, filter capacitor WE1, and load EL1.

A1	SFP port	SFP Модуль 100BASE-FX	M14.X1:TX M14.X1:RX
	SFP port	SFP Модуль 100BASE-FX	M14.X2:TX M14.X2:RX
	SFP port	SFP Модуль 100BASE-FX	M14.X3:TX M14.X3:RX
	SFP port	SFP Модуль 100BASE-FX	M14.X4:TX M14.X4:RX

The diagram shows a fiber optic connection between two A1 units. On the left, an A1 unit contains an RS-485 module and an M14.X5:RJ45 module. On the right, an A1.1 unit contains an X3:RJ45 module and an RS-485 module. The two units are connected via a fiber optic cable labeled WE3, which is terminated at both ends with 8 ohm terminators.

№	Наименование	Состояние	Наименование состояния индикации
1	Управление ИЗУ	0	Дистанционное
		1	Местное
2	Группа уставок	—	—
		—	—
3	ДЗ0	0	Введено
		1	Блокировано
4	Режим блокировки ДЗ0	0	Блокирование
		1	Сигнализация
5	Очувствление	0	Выведено
		1	Введено
6	Запрет АПВ	0	Выведено
		1	Введено
7...16	Резерв	0	Резерв
		1	Резерв
С	Сброс	0	Выведено
		1	Введено
※	Опробование световой индикации	0	Выведено
		1	Введено

№	Наименование	Режим фиксации события	Примечание
1	Внешнее отключение	с фиксацией	
2	Срабатывание ДЗО	с фиксацией	
3	Сраб. при опрб. В1	с фиксацией	
4	Сраб. при опрб. В2	с фиксацией	
5	Неисправность ЦТ	с фиксацией	
6	Неисправность ЦН	с фиксацией	
7	Выходные цепи разобраны	без фиксации	
8	БИ выведены	без фиксации	
9...16	Резерв	Резерв	

The diagram illustrates the internal wiring of the A1 module, organized into several functional blocks:

- SA1-SA10:** A series of 10 switch modules. Each module (SA1-SA9) has three terminals labeled 'Вход' (Input), 'Ряд' (Row), and 'Выход' (Output). SA10 has two terminals labeled 'Вход' and 'Выход'. The output of each switch is connected to a corresponding output terminal (e.g., 17, 5, 18 for SA1).
- M8.XA:** A set of 8 relays (M8.XA:19 to M8.XA:32). Each relay is connected to a specific input terminal (e.g., 17, 5, 18 for M8.XA:19) and an output terminal (e.g., 18, 6, 10 for M8.XA:19). The relays are labeled with 'I_A B4', 'I_B B4', 'I_C B4', and 'U_{резерв}'.
- M7.XB:** A set of 16 relays (M7.XB:3 to M7.XB:16). Each relay is connected to a specific input terminal (e.g., 17, 5, 18 for M7.XB:3) and an output terminal (e.g., 18, 6, 10 for M7.XB:3). The relays are labeled with 'I_A B4', 'I_B B4', 'I_C B4', and 'U_{резерв}'.
- M1.XP:** A set of 18 relays (M1.XP:1 to M1.XP:18). Each relay is connected to a specific input terminal (e.g., 17, 5, 18 for M1.XP:1) and an output terminal (e.g., 18, 6, 10 for M1.XP:1). The relays are labeled with 'I_A B4', 'I_B B4', 'I_C B4', and 'U_{резерв}'.
- K39-K48:** A set of 8 indicator lamps (K39 to K48). Each lamp is connected to a specific input terminal (e.g., 17, 5, 18 for K39) and an output terminal (e.g., 18, 6, 10 for K39). The lamps are labeled with 'I_A B4', 'I_B B4', 'I_C B4', and 'U_{резерв}'.
- KD2:** A set of 2 indicator lamps (KD2). Each lamp is connected to a specific input terminal (e.g., 17, 5, 18 for KD2) and an output terminal (e.g., 18, 6, 10 for KD2). The lamps are labeled with 'I_A B4', 'I_B B4', 'I_C B4', and 'U_{резерв}'.