

Цепи сигнализации

Шунки цепей сигнализации

Вызов

Неисправность терминала + неисправность защит

Срабатывание защит

Цепи РАС

The diagram illustrates the RAS (Remote Alarm Signal) circuits for two types of faults: terminal faults and protection faults. It is organized into two main sections, each with three channel configurations (A1, A2, A3).

Top Section: Неисправность терминала + неисправность защит (Terminal Fault + Protection Fault)

- Channel A1:** The "Неисправность" (Fault) signal is connected to terminal KD1. The "Неисправность защит" (Protection Fault) signal is connected to terminal M1.XP:4. The outputs of KD1 and M1.XP:4 are connected to the "X:289" terminal.
- Channel A2:** Similar to A1, with "Неисправность" at KD1 and "Неисправность защит" at M1.XP:4, connected to "X:289".
- Channel A3:** Similar to A1, with "Неисправность" at KD1 and "Неисправность защит" at M1.XP:5, connected to "X:289".

Bottom Section: Срабатывание защит (Protection Fault)

- Channel A1:** The "Срабатывание" (Trip) signal is connected to terminal KD4. The "Срабатывание защит" (Protection Trip) signal is connected to terminal M1.XP:14. The outputs of KD4 and M1.XP:14 are connected to the "X:290" terminal.
- Channel A2:** Similar to A1, with "Срабатывание" at KD4 and "Срабатывание защит" at M1.XP:15, connected to "X:290".
- Channel A3:** Similar to A1, with "Срабатывание" at KD4 and "Срабатывание защит" at M1.XP:16, connected to "X:290".

The diagram shows the internal wiring and terminal connections for these RAS circuits, with specific terminal labels like X:289 and X:290 indicating the output points for the alarm signals.

Цени портів зв'язи термінала

A1

SFP port	SFP Модуль 100BASE-FX	M14.X1:TX
		M14.X1:RX
SFP port	SFP Модуль 100BASE-FX	M14.X2:TX
		M14.X2:RX
SFP port	SFP Модуль 100BASE-FX	M14.X3:TX
		M14.X3:RX
SFP port	SFP Модуль 100BASE-FX	M14.X4:TX
		M14.X4:RX

A2

SFP port	SFP Модуль 100BASE-FX	M14.X1:TX
		M14.X1:RX
SFP port	SFP Модуль 100BASE-FX	M14.X2:TX
		M14.X2:RX
SFP port	SFP Модуль 100BASE-FX	M14.X3:TX
		M14.X3:RX
SFP port	SFP Модуль 100BASE-FX	M14.X4:TX
		M14.X4:RX

A3

SFP port	SFP Модуль 100BASE-FX	M14.X1:TX
		M14.X1:RX
SFP port	SFP Модуль 100BASE-FX	M14.X2:TX
		M14.X2:RX
SFP port	SFP Модуль 100BASE-FX	M14.X3:TX
		M14.X3:RX
SFP port	SFP Модуль 100BASE-FX	M14.X4:TX
		M14.X4:RX

Цепи портовъ свързани терминала

The diagram illustrates three terminal connection chains, labeled A1, A2, and A3 on the left, and A1.1, A2.1, and A3.1 on the right. Each chain consists of a main terminal block and a sub-terminal block. The main terminal block contains an RS-485 interface and an M14.X5RJ45 connector. The sub-terminal block contains an X3RJ45 connector and an RS-485 interface. The chains are connected by a central line with a diagonal break, labeled WE5, WE6, and WE7 respectively. The connection is shown with a double-headed arrow and a break symbol (two parallel lines with a gap).

Цепи освещения шкафа

The diagram illustrates the wiring for the cabinet lighting. A power source of $\approx 220\text{ B}$ is connected to terminals X:294, X:295 and X:296, X:297. The circuit branches into two parallel paths, EL1 and EL2. Each path contains a switch (SQ1, SQ3) and a lamp (WE1, WE3 in series with WE2, WE4). The wiring is as follows:

- Line 1 (X:294, X:295) connects to the common terminal (11) of switches SQ1 and SQ3.
- Line 2 (X:296, X:297) connects to the common terminal (21) of switches SQ1 and SQ3.
- Switch SQ1 controls lamp WE1 (terminal 12 to WE1, WE1 to terminal 22).
- Switch SQ3 controls lamp WE3 (terminal 12 to WE3, WE3 to terminal 22).
- Terminals 22 of both switches are connected to a common return line.